

Experimental General Physics for Engineers II

**Laboratory Report** PHYS 194 summer 2022

Section: \_\_L01\_\_

Experiment name:

## Transformers

Student Name:	Talha Abdullah Punjabi	Student ID	201903446
---------------	------------------------	------------	-----------

Date submitted:	15/6/2022
-----------------	-----------

---

Table of results (1.25 pts)	
Graph (1.25 pts)	
Data analysis (2 pts)	
Discussion (0.5 pt)	
References	
Others	
<b>Report Grade (5 pts)</b>	

## 1. Results

### 1.1. Geometry of the coils

Number of turns  $n$  of the primary coil:  $n_p = 300$  turns

Number of turns  $n_s$  of the secondary coil:  $n_s = 600$  turns

Which type of transformers you are using

Step up transformer

### 1.2. Efficiency as a function of load


$R_L (\Omega)$	$u(R_L) (\Omega)$	$V_p$ (volt)	$u(V_p)$ (volt)	$I_p$ (A) (ampere)	$u(I_p)$ (A) (ampere)	$V_s$ (volt)	$u(V_s)$ (volt)	$I_s$ (A) (ampere)	$u(I_s)$ (A) (ampere)
5	$\pm 0.05$	6.97	$\pm 0.01$	0.6877	$\pm 0.0001$	2.15	$\pm 0.01$	0.3292	$\pm 0.0001$
20	$\pm 0.2$	6.90	$\pm 0.01$	0.5942	$\pm 0.0001$	5.72	$\pm 0.01$	0.2780	$\pm 0.0001$
40	$\pm 0.4$	6.91	$\pm 0.01$	0.4718	$\pm 0.0001$	8.71	$\pm 0.01$	0.2162	$\pm 0.0001$
80	$\pm 0.8$	6.74	$\pm 0.01$	0.3230	$\pm 0.0001$	11.18	$\pm 0.01$	0.1413	$\pm 0.0001$
120	$\pm 1.2$	7.03	$\pm 0.01$	0.2439	$\pm 0.0001$	12.15	$\pm 0.01$	0.1014	$\pm 0.0001$
140	$\pm 1.4$	7.05	$\pm 0.01$	0.2194	$\pm 0.0001$	12.41	$\pm 0.01$	0.0890	$\pm 0.0001$
160	$\pm 1.6$	7.06	$\pm 0.01$	0.2003	$\pm 0.0001$	12.60	$\pm 0.01$	0.0792	$\pm 0.0001$
200	$\pm 2.0$	7.08	$\pm 0.01$	0.1720	$\pm 0.0001$	12.87	$\pm 0.01$	0.0647	$\pm 0.0001$
280	$\pm 2.8$	7.11	$\pm 0.01$	0.1394	$\pm 0.0001$	13.15	$\pm 0.01$	0.0475	$\pm 0.0001$

$R_L (\Omega)$	$P_{in}$ (watts)	$u(P_{in})$ (watts)	$P_{out}$ (watts)	$u(P_{out})$ (watts)	$\eta$	$u(\eta)$
5	4.79	$\pm 0.007$	0.708	$\pm 0.003$	0.147	$\pm 0.002$
20	4.10	$\pm 0.006$	1.590	$\pm 0.003$	0.387	$\pm 0.004$
40	3.26	$\pm 0.005$	1.883	$\pm 0.002$	0.577	$\pm 0.006$
80	2.17	$\pm 0.003$	1.580	$\pm 0.002$	0.725	$\pm 0.008$
120	1.71	$\pm 0.002$	1.232	$\pm 0.001$	0.718	$\pm 0.009$
140	1.55	$\pm 0.002$	1.104	$\pm 0.001$	0.714	$\pm 0.009$

0	1.41	$\pm 0.002$	0.997	$\pm 0.001$	0.705	$\pm 0.010$
200	1.22	$\pm 0.001$	0.833	$\pm 0.001$	0.683	$\pm 0.010$
280	0.99	$\pm 0.001$	0.625	$\pm 0.001$	0.630	$\pm 0.011$
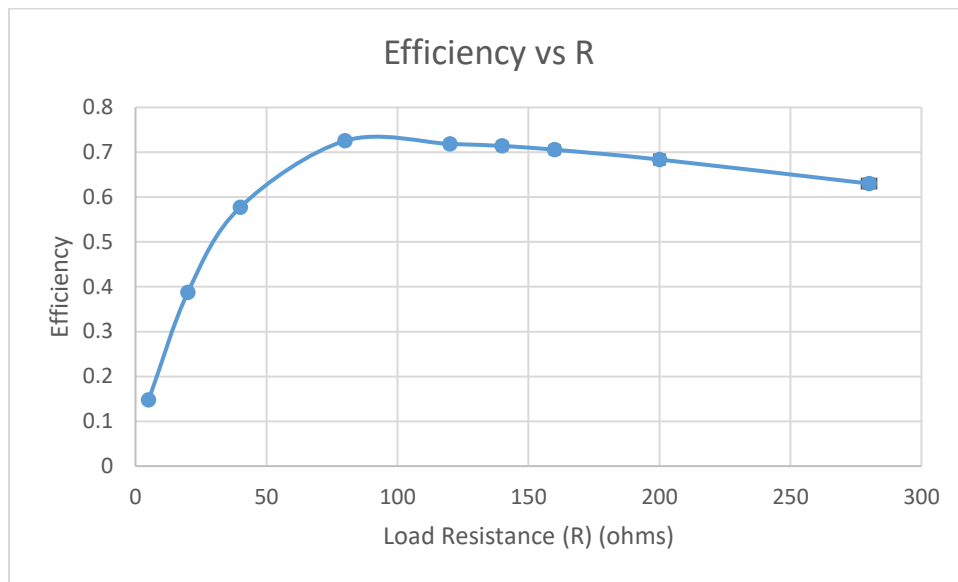
### 1.3. Graph $\eta$ vs. $R_L$

Plot  $\eta$  vs.  $R_L$  in Excel with error bars



### 1.4. Uncertainty on $P_{in}$ , $P_{out}$ and $\eta$

Show how you calculate  $u(P_{in})$ ,  $u(P_{out})$ ,  $u(\eta)$

$$P_{in} = V_p * I_p$$

$$U(P_{in}) = \sqrt{((d(V_p * I_p)/d(V_p) * U(V_p))^2 + (d(V_p * I_p)/d(I_p) * U(I_p))^2)}$$

$$= \sqrt{((I_p * U(V_p))^2 + (V_p * U(I_p))^2)}$$

$$= \sqrt{((0.01 * 0.6877)^2 + (0.0001 * 6.97)^2)}$$

$$= \pm 0.0069 \text{ watts}$$

$$U(P_{in}) = \sqrt{((d(V_s * I_s)/d(V_s) * U(V_s))^2 + (d(V_s * I_s)/d(I_s) * U(I_s))^2)}$$

$$= \sqrt{((I_s * U(V_s))^2 + (V_s * U(I_s))^2)}$$

$$= \sqrt{((0.01 * 0.3292)^2 + (0.0001 * 2.15)^2)}$$

$$= \pm 0.0033 \text{ watts}$$

$$U(\eta) = \sqrt{\left(\frac{d(P_{out}/P_{in})}{d(P_{out})} * U(P_{out})\right)^2 + \left(\frac{d(P_{out}/P_{in})}{d(P_{in})} * U(P_{in})\right)^2}$$

$$= \sqrt{\left(\frac{U(P_{out})}{P_{in}}\right)^2 + (-P_{out} * P_{in}^{-2} * U(P_{in}))^2}$$

$$= \sqrt{(0.0033/4.79)^2 + (-0.7078 * 4.79^{-2} * 0.0069)^2}$$

$$= \pm 0.0026$$

### 1.5. Maximum efficiency

Find the load resistance for which efficiency is maximum

By observing the table and the graph, we see that maximum efficiency was at when the load resistance was **80  $\Omega$**  where the efficiency was **72.5%**

### 2. Discussion

The experiment was successful and the results whereas it was expected. Firstly, we increase the load resistance and note the efficiency which kept on increasing reaching its maximum at 72.5% efficiency while load was 80  $\Omega$ . After that efficiency start decreasing with the increase in load resistance.

Possible sources of error could be human error while building up the connections that is machine errors and inaccuracy while noting the values.

### 3. References